

## ***LAB-3 Various CMOS Logic Families***

Based on XOR circuit, analyze the circuit characteristics of three different Logic Families:

1. Observe the performance results in terms of power, delay, and pdp when the circuit is faced with **different loadings** under a fixed size.
2. Observe the performance results of **different circuits** in terms of power, delay, and pdp.

Using the same test pattern:


```
va  a  0  pulse(1.8 0  0.1n  0.1n  0.1n  39.9n  80n)
vb  b  0  pulse(1.8 0  0.1n  0.1n  0.1n  79.9n  160n)
vc  c  0  pulse(1.8 0  0.1n  0.1n  0.1n  159.9n  320n)
.tran  0.1n  640n
```

### LAB3-1 : Static CMOS 3-input XOR (25%)

Write 3-input Static CMOS XOR SPICE, observe the waveform and measure Delay time , Power consumption , Power-Delay-Product .

1. Size:  $L=0.18\mu$ ,  $W$ : Please size it according to the figure below.
2. Using fixed loading capacitance  $c=0.05p$
3. **(extra practice)** Modify your input pattern with 2 times, 4times ,8 times, and 16times frequency (Record the Delay time and Power consumption according to Frequency changes in Excel.)

Static CMOS 3-input XOR :

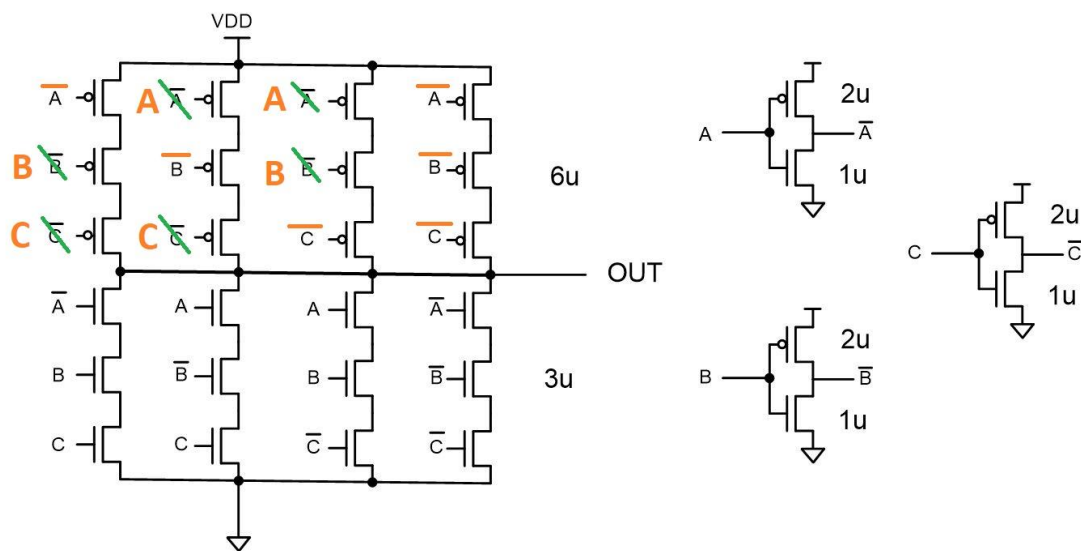


## LAB3-2 : **Pseudo-NMOS 3-input XOR** (25%)

Write 3-input Pseudo NMOS CMOS XOR SPICE, observe the waveform and measure Delay time , Power consumption , Power-Delay-Product .

1. Size:  $L=0.18\mu$ ,  $W$ : Please size it according to the figure below.
2. Using fixed loading capacitance  $c=0.05p$
3. **(extra practice)** Modify your input pattern with 2 times, 4times ,8 times, and 16times frequency (Record the Delay time and Power consumption according to Frequency changes in Excel.)

Pseudo-NMOS 3-input XOR :

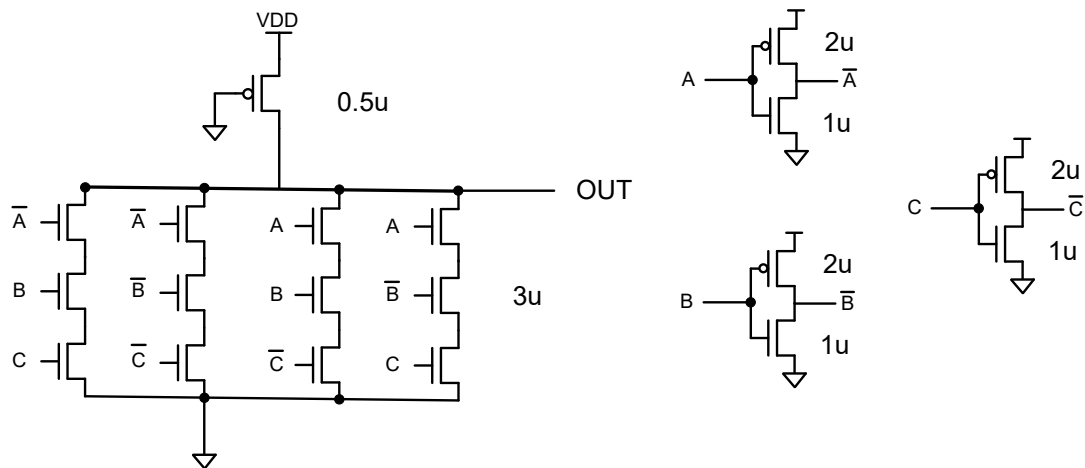

### LAB3-3 : **Pass-transistor 3-input XOR** (25%)

Write 3-input Pass-transistor CMOS XOR SPICE, observe the waveform and measure Delay time , Power consumption , Power-Delay-Product .

1. Size:  $L=0.18\mu$ ,  $W$ : Please size it according to the figure below.
2. Using fixed loading capacitance  $c=0.05p$
3. **(extra practice)** Modify your input pattern with 2 times, 4times ,8 times, and 16times frequency (Record the Delay time and Power consumption according to Frequency changes in Excel.)

Pass- transistor 3-input XOR :

