

LAB-2 Scaling Property


1. Discuss how do fan-in, fan-out, and cascade stage affect delay and power?

*The Pattern you need:

Please test with the following pattern:

(To see how many patterns you need, ex: two inputs with va and vb, four inputs with va, vb, vc, and vd.)

 
Note: Please put input A to the MOS transistor most near VDD or GND.



VA	A	0	pulse(1.8	0	0.1n	0.1n	0.1n	9.9n	20n)
VB	B	0	1.8						
VC	C	0	1.8						
VD	D	0	1.8						
VE	E	0	1.8						
VF	F	0	1.8						
VG	G	0	1.8						
VH	H	0	1.8						
.tran	0.1n	80n							

Analysis of NAND fan-in, fan-out, and cascade-stage

 1. Please Analysis and compare the 2-input NAND, 4-input NAND, 6-input NAND, 8-input NAND circuits under various fan-in with the same **loading $c=0.02p$** . Please measure Delay time and Power consumption with transistor Size using PMOS $W/L=1u/0.18u$, NMOS $W/L=1u/0.18u$. (Using EXCEL to record Delay and Power according to various fan-in change.)
2. Please Analysis and compare the 4-input NAND, under various fan-out with **loading $c=0.05p, 0.1p, 0.15p, 0.2p, 0.25p, \dots, 1p$** . Please measure Delay time and Power consumption with transistor Size using PMOS $W/L=1u/0.18u$, NMOS $W/L=1u/0.18u$. (Using EXCEL to record Delay and Power according to various fan-out change.)
3. Please cascade the 2-input NAND as following, with fan-out loading $c=0.02p$. Please measure Delay time and Power consumption with transistor Size using PMOS $W/L=1u/0.18u$, NMOS $W/L=1u/0.18u$. (Using EXCEL to record Delay and Power according to various cascade stage change.)



2-input NAND Cascade